

The MD-2 PC Board

The job of the MD-2 board is to convert swell shoe movement into the appropriate electrical signals. This page describes how it works and what it does.

Keep in mind that the MD-2 program is easily changeable, and can be adapted to many different purposes. In my organ I have two swell shoes, which will use two MD-2 boards. At this point I am planning to use one for each keyboard, but I may at some point decide to use one of these as a crescendo pedal.

Swell Shoe Sensor

In the original Schober organs, the swell shoe controlled a potentiometer ("pot") through a rack-and-pinion gear arrangement. In early organs this pot directly controlled the volume, but after some time this developed a problem --- the pot would become noisy and introduce crackling into the audio. Schober thus redesigned the circuit: the pot would control the intensity of a light bulb, the bulb would shine on a cadmium sulfide cell, the cell's resistance would change with the light intensity, and this would be used to control the volume. The advantage of this system is that the thermal inertia of the lamp causes just enough delay to smooth out any irregularities.

I've replaced the potentiometer with a digital rotary encoder, shown in the photo. The encoder is a three-terminal device which acts like a pair of switches that alternately open and close as the encoder shaft is turned. As you turn the shaft, the switches operate like this:

<u>Switch B</u>	<u>Switch A</u>
open	open
open	close
close	close
close	open
open	open
etc. etc.	

In other words, both switches start open. After a tiny turn, switch A closes. A slight turn further and B closes. Another slight turn and A opens, and then a bit later B also opens. This repeats, over and over, a total of 24 times over one 360-degree revolution. (For digital freaks, this is called a 2-bit Gray code.) If the encoder shaft turns in the opposite direction, the sequence is reversed.



The advantage of this scheme is that if the switches age and become intermittently noisy, the digital effect is minimal. The encoders I chose cost about \$2 each and are guaranteed for 10,000 revolutions (they are part number 318-ENC160-24P from Mouser Electronics, a Taiwan Alpha Rotary Encoder model RE160-40E3-20A-24P). If that isn't good enough, I can always replace them with \$70 encoders which use optics instead of physical switches and which are guaranteed for something like 10 million revolutions. (There are several other mechanical encoders in the Mouser catalog as well.)

But there is also a disadvantage. Since the two-bit code repeats over and over, the system can recognize tiny swell shoe movement, but it can't be sure exactly how far the swell shoe pedal is depressed. My software will require a learning sequence - when you first turn the organ on, regardless of where the swell shoe is actually positioned, the MD-2 board will assume that it is at minimum volume. The organist will have to do one complete top-to-bottom-to-top movement so that the MD-2 software can learn what the maximum and minimum settings are. After that, it will figure out the current position by keeping track of the history of up and down motions.

MD-2 function

Swell shoe sensor position is monitored by a 68HC11 microprocessor; its circuitry is very similar to the MD-1 board, and is explained later. The processor keeps track of swell shoe position and does three things each time it senses that the swell shoe has been moved:

1. It outputs a MIDI controller message via its 5-pin MIDI OUT connector. The channel number is set by a four-pole DIP switch, similar to that on the MD-1 board.
2. It outputs a 7-bit code out the 9-pin serial connector. A serial cable sends this code to the MD-1 board. The MD-1 program accepts this number and uses it as the velocity byte in current note-on messages.
3. The MD-2 board also has space for a PGA2310PA audio integrated circuit. This is a dual volume control (for stereo applications) which is controlled digitally by the microprocessor. This allows me to directly control audio volume for other signal sources.

My main organ tone generator is either the Hauptwerk program, or the Kloria MyOrgan program; both of these use samples of real organ pipes. These two programs both accept MIDI controller messages, but Hauptwerk ignores velocity commands. (I don't yet know about MyOrgan.)

My secondary tone source is a Roland CM32P. This is a MIDI tone module which uses short samples to play sounds. It has a number of sounds, but I anticipate using only the piano in conjunction with Hauptwerk's theatre organ samples. This module uses the velocity code in note-on messages.


At this point I don't see the need for an audio volume control so, although the MD-2 board has space for the PGA2310PA audio volume control, that part of the boards is not populated, nor have I written the software for that function.

MD-2 Circuitry

The MD-2 board is divided into two parts --- the digital side on the left, and the analog side on the right. To prevent the digital control signals or noise from getting into the analog circuits, the two sides use separate grounds and separate power supplies for isolation. The digital side is shown in Figure 1, while the analog side is in Figure 2.

Digital circuitry

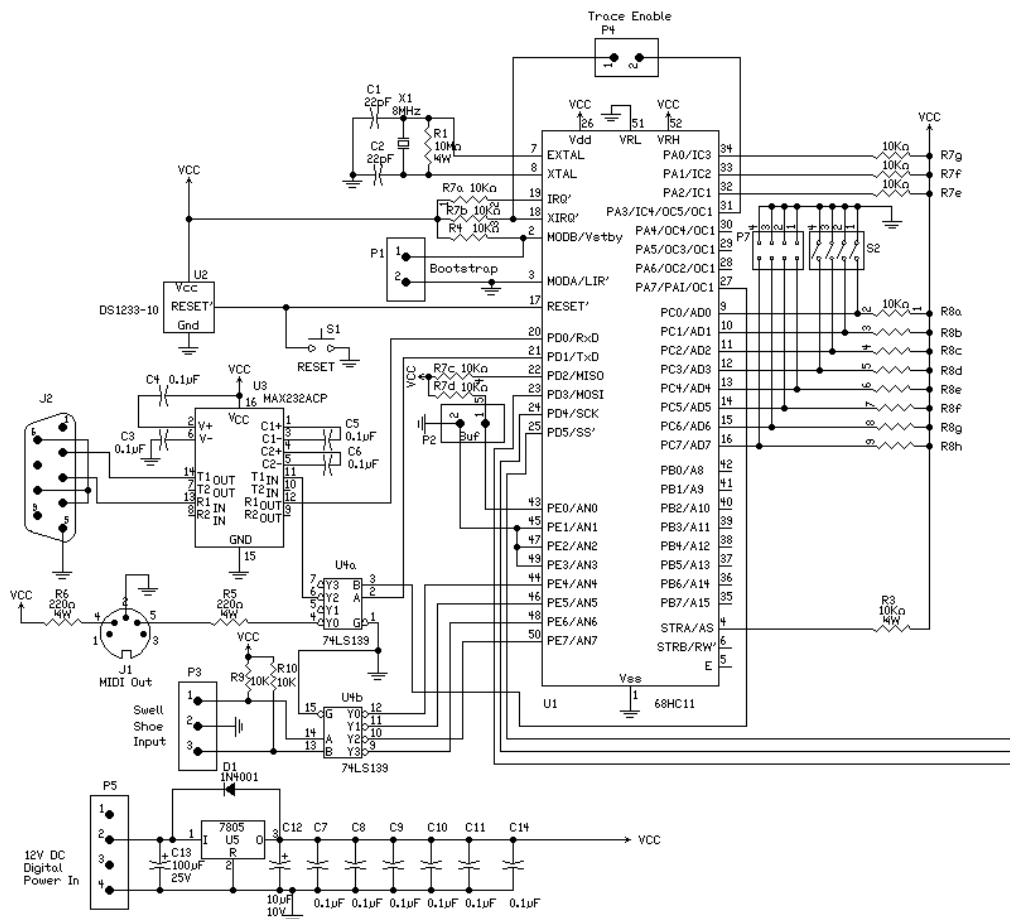The digital circuit in Figure 1 is actually very similar to the MD-1 board.



(a) Top left is the 8 MHz crystal and attached circuitry, which sets the speed of the processor. The 68HC11 internally divides this by 4, so the main clock frequency of the processor is 2 MHz.


(c) Jumper P1 allows bootstrapping the HC11. In normal mode, this jumper would be open. When pins 1 and 2 of the jumper are shorted together, the processor goes into a bootstrap mode, where it can be loaded with a program through the serial port. This is the method that the EEPROM software would initially be loaded.

(e) The 68HC11 has a built-in serial I/O port which can run at the standard baud rates, as well as at 31.25 kHz, the MIDI rate. It uses pins 20 and 21. This serial port connects both to 9-pin RS-232 connector J2, and also to MIDI OUT jack J1.

- There is 9-pin DB9F connector, which can be connected to the comm port of a PC. It does two jobs: (1) During program development, it is used for loading the software into the processor, and also for program testing. (2) During operation, it outputs velocity information which is sent to the corresponding MD-1 board. The MAX232 IC, U3, is used as the converter between the low-level TTL voltages used by the HC11, and the positive and negative larger voltages used by typical RS-232 ports at the DB9F connector. It includes a charge pump which provides the necessary +10 and -10 power for output).

Serial output from U1 pin 21 goes through U4a, a 74LS139. I'm using it to steer the output to either the MAX232 or the MIDI jack. It is controlled by its B input pin, which comes from pin 27 of the HC11 - it is normally held high on CPU reset, so the normal connection is to the 9-pin connector. If the 68HC11 wants to output MIDI, it grounds this B input (via U1 pin 27), and changes the baud rate to 31.25 kHz.

 (f) Jumpers P2 and P4 are left open in organ applications, but they allow this board to run with the Motorola Buffalo version of the 68HC11 for debugging purposes. P2 selects whether the Buffalo program will run, or whether the HC11 will instead jump to location B600 on bootup. P4 is used to enable tracing and breakpoints. As mentioned, these two jumper headers are here strictly for debugging and other applications.




(i) Connector pins P7 provide four auxiliary inputs "just in case".


The circuit diagram illustrates a 12V AC to 0V-5V analog signal converter. It features a central PGA2310 (U6) which is configured as a differential line driver. The input stage consists of a 12V AC source connected to a bridge rectifier (D2, D3, D4, D5) and a voltage divider (R1, R2). The rectified signal is then filtered by a 470µF capacitor (C21) and a 25V Zener diode (U8) to provide a stable reference. The PGA2310's inputs are connected to the filtered signal and a reference voltage. The output stage uses two NE5532 op-amp buffers (U9a, U9b) to drive the VA+ and VA- signals. The circuit is powered by a 12V supply (VCC) and includes various passive components like resistors (R1-R17), capacitors (C1-C28), and diodes (D1-D5) for signal conditioning and protection.

PCB Layout

The top solder side:

 
 
<http://www.users.cloud9.net/~stark/md2.htm>



THE SOFTWARE

The 68HC11A1 has 512 bytes of EEPROM and 256 bytes of RAM, and only about 50% of each is used in the program. Here is the listing for version 1.0.

```

0001      * MD-2 Swell Shoe program
0002      * Copyright (C) 2006 by Peter A. Stark
0003
0004      * Version 1.0 8/29/2006 - original
0005      * THIS VERSION ONLY OUTPUTS SERIAL OUTPUT ON RS-232 AND MIDI
0006      * AUDIO VOLUME CONTROL IS NOT IMPLEMENTED
0007
0008      * I/O bits:
0009      *   Inputs
0010      * PD0: Serial RS232 input from J2
0011      * PC3-0: Channel DIP switch S2
0012      * PC7-4: extra inputs on P7
0013      * PE0: Jumper to ground for Buffalo P2
0014      * PE7-4: Rotary encoder signal from P3
0015      * MODB: Bootstrap mode jumper P1
0016      * XIRQ': Trace enable from P4
0017
0018      *   Outputs
0019      * PA7: H=RS232 (default), L=MIDI out
0020      * PD1: Serial out to RS232 or MIDI to J2
0021      * PD5-3: SS', SCK, MOSI to PGA2310
0022
0023
0024      *****
0025      *   GENERAL SYSTEM EQUATES
0026      *****
0027
0028 0000      RAM      EQU    $0000      START OF RAM
0029 1000      REG      EQU    $1000      START OF REGISTERS
0030 b600      EEPROM   EQU    $B600      START OF EEPROM
0031 b7ff      ENDEEP   EQU    $B7FF      END OF EEPROM
0032 1000      PORTA    EQU    $1000      PORT A DATA & TIMER - B7=BI, B6-3=O,B2-1=I
0033 1026      PACTL    EQU    $1026      PORT A CONTROL
0034 1004      PORTB    EQU    $1004      PORT B DATA - OUTPUT ONLY
0035 1003      PORTC    EQU    $1003      PORT C DATA - BI
0036 1005      DDRC     EQU    $1005      PORT C DIRECTION
0037 1008      PORTD    EQU    $1008      PORT D DATA - 6 BITS BI & SCI/SPI
0038 1009      DDRD     EQU    $1009      PORT D DIRECTION
0039 100a      PORTE    EQU    $100A      PORT E - INPUT ONLY & A/D
0040 102b      BAUD     EQU    $102B      SCI BAUD REG
0041 102c      SCCR1    EQU    $102C      SCI CONTROL 1 REG
0042 102d      SCCR2    EQU    $102D      SCI CONTROL 2 REG
0043 102e      SCSR     EQU    $102E      SCI STATUS REG
0044 102f      SCDAT    EQU    $102F      SCI DATA REG
0045 1028      SPCR     EQU    $1028      SPI CONTROL REG
0046 1029      SPSR     EQU    $1029      SPI STATUS REG
0047 102a      SPDR     EQU    $102A      SPI DATA REG
0048 103a      COPRST   EQU    $103A      COP RESET REG
0049 000b      BXCONT   EQU    11        CONTROLLER CHANNEL = 11
0050
0051      *****
0052      *   RAM LOCATIONS
0053      *****
0054
0055 0000      ORG      RAM
0056
0057      * SET UP A CIRCULAR SERIAL OUTPUT BUFFER
0058      * CAUTION - BUFFER MUST START AT $0000 !

```

```

0059      * EMPTY IF BUFIN=BUFOUT, DON'T WORRY ABOUT FULL -
0060      * HOPEFULLY WILL NEVER HAPPEN
0061 0000      BUFFER   RMB    64    SERIAL OUTPUT BUFFER
0062 0040      BUFIN    RMB     2    PUT NEXT BYTE HERE POINTER
0063 0042      BUFOUT   RMB     2    NEXT BYTE TO OUTPUT POINTER
0064
0065 0044      SWSHOE   RMB     1    CURRENT SW SHOE POSITION
0066 0045      STAPOS   RMB     1    SHOE STARTING POSITION
0067 0046      PREVSH   RMB     1    PREVIOUS POSITION
0068 0047      VOLUME   RMB     1    CURRENT VOLUME
0069 0048      TIVOL    RMB     1    VOLUME DOCTORED UP FOR TI CHIP
0070 0049      RSVOL    RMB     1    VOLUME DOCTORED UP FOR RS-232 OUTPUT
0071 004a      BXVOL    RMB     1    VOLUME FOR BX CONTROL CHGE MSG
0072 004b      BXCHAN   RMB     1    BX + CHANNEL NUMBER
0073
0074 007f      STACK    EQU     $007F
0075
0076      *****
0077      * Start and Initialize ports
0078      *****
0079
0080 b600              ORG     EEPROM
0081
0082 b600 8e 00 7f      COLDST  LDS     #STACK
0083 b603 7f 10 04              CLR     PORTB      OUTPUT - NOT USED
0084 b606 7f 10 05              CLR     DDRC      PORT C IS ALL INPUT
0085 b609 86 38              LDAA    #$38      PORT D IS INPUT EXC SERIAL...
0086 b60b b7 10 09              STAA   DDRD      ...AND SPI OUTPUT
0087 b60e 7f 10 0a              CLR     PORTE      PORT E IS ALL INPUT
0088
0089      *****
0090      *   Initialize the SCI serial port
0091          use $30 for 9600 baud during testing
0092      *   use $20 for 31.25K baud for final version
0093      *****
0094 b611 ce 10 00              LDX     #REG      POINT TO REGISTERS
0095 b614 1c 00 80              BSET    PORTA-$1000,X $80 PA7=H FOR RS232
0096 b617 1c 26 80              BSET    PACTL-$1000,X $80 ... AND OUTPUT
0097 b61a 86 20              LDAA    #$20      SET 9600 BAUD TEMPORARY
0098 b61c b7 10 2b              STAA   BAUD      BAUD REGISTER
0099 b61f 86 00              LDAA    #$00      SET 8X1, NO WAKEUP
0100 b621 b7 10 2c              STAA   SCCR1
0101 b624 86 0c              LDAA    #$0C
0102 b626 b7 10 2d              STAA   SCCR2      ENABLE
0103
0104      *****
0105      *   Initialize SPI port not needed until we add audio control
0106      *****
0107
0108
0109      *****
0110      *   WARMST - WARM START
0111      *****
0112
0113 b629 b6 10 03      WARMST  LDAA    PORTC      GET CHANNEL NUMBER
0114 b62c 84 0f              ANDA    #$0F      MASK IT
0115 b62e 8b b0              ADDA    #$B0      MAKE INTO CTRL CHG COMMAND
0116 b630 97 4b              STAA   BXCHAN
0117 b632 7f 00 47              CLR     VOLUME      INITIAL = 0
0118 b635 7f 00 45              CLR     STAPOS      STARTING POSITION = 0
0119 b638 86 04              LDAA    #4
0120 b63a 97 46              STAA   PREVSH      PREV POSITION = 4
0121 b63c 4f              CLRA
0122 b63d 5f              CLR    B
0123 b63e dd 40              STD     BUFIN      BUFFER IS EMPTY
0124 b640 dd 42              STD     BUFOUT
0125
0126 b642 86 55      MAINLP   LDAA    #$55
0127 b644 b7 10 3a              STAA   COPRST      RESET COP TIMER
0128 b647 86 aa              LDAA    #$AA      JUST IN CASE
0129 b649 b7 10 3a              STAA   COPRST
0130
0131 b64c b6 10 0a              LDAA    PORTE      GET DATA
0132 b64f 43              COMA
0133 b650 44              LSRA
0134 b651 44              LSRA
0135 b652 44              LSRA
0136 b653 44              LSRA
0137 b654 97 44              STAA   SWSHOE
0138 b656 90 46              SUBA   PREVSH      SUBTRACT PREVIOUS
0139 b658 27 6a              BEQ    OUTPUT      NO CHANGE
0140
0141      * FIGURE OUT IF UP OR DOWN
0142 b65a 81 07              CMPA   #$7          DOWN CUR=8 PREV=1
0143 b65c 27 0e              BEQ    DOWN
0144 b65e 81 f9              CMPA   #$F9         UP CUR=1 PREV=8
0145 b660 27 05              BEQ    UP

```

```

0146 b662 4d          TSTA
0147 b663 2a 02      BPL UP
0148 b665 2b 05      BMI DOWN
0149
0150 b667 7c 00 45    UP      INC STAPOS
0151 b66a 20 05      BRA OK
0152
0153 b66c 7a 00 45    DOWN    DEC STAPOS
0154 b66f 20 00      BRA OK
0155
0156 b671 96 44      OK      LDAA SWSHOE      GET CURRENT POSITION
0157 b673 97 46      STAA PREVSH    SAVE AS PREVIOUS
0158 b675 81 04      CMPA #$04      ON INDENT?
0159 b677 26 4b      BNE OUTPUT    NO, SO CONTINUE
0160
0161
0162
0163
0164 b679 96 45      LDAA STAPOS
0165 b67b 27 47      BEQ OUTPUT    JUST IGNORE IF NO CHANGE
0166 b67d 7f 00 45    CLR STAPOS    CLEAR IT FOR NEXT
0167 b680 4d          TSTA
0168 b681 2a 08      BPL INCVOL    INCREASE VOLUME IF +
0169
0170
0171 b683 96 47      * DECREASE VOLUME IF -, BUT NOT BELOW 0
0172 b685 4a      DECVOL LDAA VOLUME
0173 b686 2a 0c      DECA
0174 b688 4f      BPL VOLOK
0175 b689 20 09      CLRA
0176
0177
0178 b68b 96 47      * INCREASE VOLUME IF +, BUT NOT ABOVE 20
0179 b68d 4c      INCVOL LDAA VOLUME
0180 b68e 81 14      INCA
0181 b690 23 02      CMPA #20
0182 b692 86 14      BLS VOLOK
0183 b694 97 47      LDAA #20
0184
0185
0186
0187 b696 96 47      VOLOK STAA VOLUME
0188 b698 48      * NOW DOCTOR UP THE VOLUME TO DESIRED RANGE ~~
0189 b699 48      LDAA VOLUME      VALUE = 0 TO 20
0190 b69a 8b 1e      LSLA
0191 b69c 97 49      ADDA #30      VALUE = 0 TO 80
0192
0193
0194
0195 b69e 97 4a      STAA BXVOL      FOR NOW USE THE SAME
0196
0197
0198
0199
0200
0201 b6a0 de 40      * NEXT OUTPUT VIA SPI PORT TO TI CHIP - USE TIVOL ~~
0202 b6a2 86 80      * PUT RSVOL STUFF INTO CIRC BUFFER
0203 b6a4 d6 49      LDX BUFIN
0204 b6a6 ed 00      LDAA #$80      OUTPUT VIA RS232
0205 b6a8 8d 3c      LDAB RSVOL      VOLUME
0206
0207
0208
0209 b6aa de 40      STD 0,X      PUT BOTH INTO BUFFER
0210 b6ac 86 00      BSR INCIN    BUMP POINTER BY 2
0211 b6ae d6 4b      LDX BUFIN
0212 b6b0 ed 00      LDAB #BXCONT  CONTROLLER NUMBER...
0213 b6b2 8d 32      STD 0,X      ...INTO BUFFER
0214 b6b4 de 40      BSR INCIN    BUMP POINTER BY 2
0215 b6b6 c6 0b      LDX BUFIN
0216 b6b8 ed 00      LDAB BXVOL    AND VOLUME...
0217 b6ba 8d 2a      STD 0,X      ...INTO BUFFER
0218 b6bc de 40      BSR INCIN    BUMP POINTER BY 2
0219 b6be d6 4a      LDX BUFIN
0220 b6c0 ed 00      LDAB BXVOL    AND VOLUME...
0221 b6c2 8d 22      STD 0,X      ...INTO BUFFER
0222
0223
0224
0225 b6c4 96 41      BSR INCIN    BUMP POINTER BY 2
0226 b6c6 91 43      * NOW OUTPUT FROM BUFFER IF NEEDED
0227 b6c8 26 03      OUTPUT LDAA BUFIN+1
0228 b6ca 7e b6 42      CMPA BUFOUT+1
0229
0230 b6cd f6 10 2e    BNE SKIP1    CONT IF NOT EMPTY
0231 b6d0 c4 40      JMP MAINLP   ELSE REPEAT LOOP
0232 b6d2 26 03      SKIP1 LDAB SCSR      READ STATUS
0233
0234
0235
0999
1000

```

```

0233 b6d4 7e b6 42          JMP    MAINLP    ...XMTR BUSY, SO REPEAT LOOP
0234
0235 b6d7 de 42          OUT2    LDX    BUFOUT
0236 b6d9 ec 00          LDD     0,X      GET TWO BYTES FROM BUFFER
0237 b6db b7 10 00      STAA    PORTA    CHOOSE RS232 IF H OR MIDI IF L
0238 b6de f7 10 2f      STAB    SCDAT    SEND CHARACTER
0239 b6e1 8d 0c          BSR     INCOUT    BUMP POINTER BY 2
0240
0241          * AND FINALLY RETURN INTO LOOP
0242
0243 b6e3 7e b6 42          JMP    MAINLP
0244
0245          * INCREMENT BUFIN POINTER BY 2
0246 b6e6 d6 41      INCIN    LDAB    BUFIN+1
0247 b6e8 5c          INCB
0248 b6e9 5c          INCB
0249 b6ea c4 3f      ANDB    #$3F      BUFFER SIZE = 64
0250 b6ec d7 41      STAB    BUFIN+1
0251 b6ee 39          RTS
0252
0253          * INCREMENT BUFOUT POINTER BY 2
0254 b6ef d6 43      INCOUT    LDAB    BUFOUT+1
0255 b6f1 5c          INCB
0256 b6f2 5c          INCB
0257 b6f3 c4 3f      ANDB    #$3F      BUFFER SIZE = 64
0258 b6f5 d7 43      STAB    BUFOUT+1
0259 b6f7 39          RTS
0260
0261
0262 b6f8 43 4f 50 59 52 49  COPRIT  FCC  'COPYRIGHT' (c) 2006 BY '
    47 48 54 20 28 63
    29 20 32 30 30 36
    20 42 59 20
0263 b70e 50 45 54 45 52 20      FCC  'PETER A. STARK'
    41 2e 20 53 54 41
    52 4b
0264
0265
0266          END

```

The above program is subject to change. Aside from the lack of PGA2310PA audio support -- which may not ever really be needed -- there may be some slight adjustments needed to provide the correct scaling for the MIDI controller output and velocity output. Right now, both of these settings range from a minimum of 30 to a maximum of 110, but this may need to be changed. See the sections identified with two tildes (~~) in the above listing.

A Note on the DIP Switch, and Jumpers

DIP switch S2 sets the channel number *minus 1*. That is, MIDI channels are numbered 1 through 16, but the binary code used is 0 through 15. For example, if I want to play on channel 13, I actually set S1 to 1100, which is the binary number for 12. The way the switches are wired, an open switch generates a 1 while a closed switch is a 0, so the four switches are set to open-open-closed-closed.

Jumpers: There are several header strips for jumpers. When using a 68HC11A1 that has Motorola's Buffalo debugger programmed into its ROM, P1, P2, and P4 determine the operating mode for the software, as follows:

1. To run Buffalo, place a shorting jumper on P2 and P4. This allows you to do various debugging functions via the serial port; if you have programmed the MD-1 software into the chip, you can do a manual jump to it at location B600.
2. To have Buffalo start, but then right away automatically jump to the MD-1 software at location B600, remove all jumpers. This is the normal operating mode once you have programmed the chip and installed the board into your organ.
3. To go into bootstrap mode, so you can program the chip via the serial port, place a shorting jumper on P1.

Location P7, right next to the DIP switch, is "for future use". It is an extra set of four inputs that can be used for other applications, if needed, but not used in this application. For example, the 4-pole DIP switch could be replaced with an 8-pole switch, with the extra four poles used for other input information.